

Appendix A

Loudspeaker dimensions.	ii.
Loudspeaker measurement chart-L\H.	iii.
Loudspeaker measurement chart-R\H.	iv.
Loudspeaker impedance curve chart-L\H.	v.
Loudspeaker impedance curve chart-R\H.	vi.
Woofer impedance calculation chart.	vii.
Woofer impedance equalizer calculation chart.	viii.
Woofer Relative efficiency calculation.	viii.
Midrange impedance calculation chart.	ix.
Midrange notch filter calculation chart.	ix.
Tweeter impedance calculation chart.	x.
Tweeter notch filter calculation chart.	x.
Crossover network calculation chart.	xi.
Multiplier table	xii.
Crossover parts list.	xiii.
Inductance chart	xiv.
Crossover schematic diagram.	xv.
Crossover layout diagram.	xvi.

Loudspeaker Dimensions

Woofer		
Outside diameter	W_{diam}mm.
Woofer radius	R_wmm.
Magnet radius	r_wmm.
Woofer height	H_wmm.
Cone depth	W_{cone}mm.
Flange thickness	W_{flange}mm.
Flange width	W_{rebate}mm.
Cut-out diameter	W_{hole}mm.
Mounting screws		M.....
Midrange		
Outside diameter	M_{diam}mm.
Tube radius	R_mmm.
Tube height	H_mmm.
Cone depth	M_{cone}mm.
Flange thickness	M_{flange}mm.
Flange width	M_{rebate}mm.
Cut-out diameter	M_{hole}mm.
Mounting screws		M.....
Tweeter		
Outside diameter	T_{diam}mm.
Magnet radius	R_tmm.
Cone depth	T_{cone}mm.
Flange thickness	T_{flange}mm.
Flange width	T_{rebate}mm.
Cut-out diameter	T_{hole}mm.
Mounting screws		M.....

Appendix A


FREQUENCY Hz.	V _S mvolts.	V _R volts.	IMPEDANCE Ohms.
10			
15			
20			
25			
30			
35			
40			
50			
60			
70			
80			
90			
100			
200			
300			
400			
500			
600			
700			
800			
900			
1000			
Resonant Frequency - F _s			

Woofer Impedance Data Chart. (Left hand)


Appendix A

FREQUENCY Hz.	V _S mvolts.	V _R volts.	IMPEDANCE Ohms.
10			
15			
20			
25			
30			
35			
40			
50			
60			
70			
80			
90			
100			
200			
300			
400			
500			
600			
700			
800			
900			
1000			
Resonant Frequency - F _s			

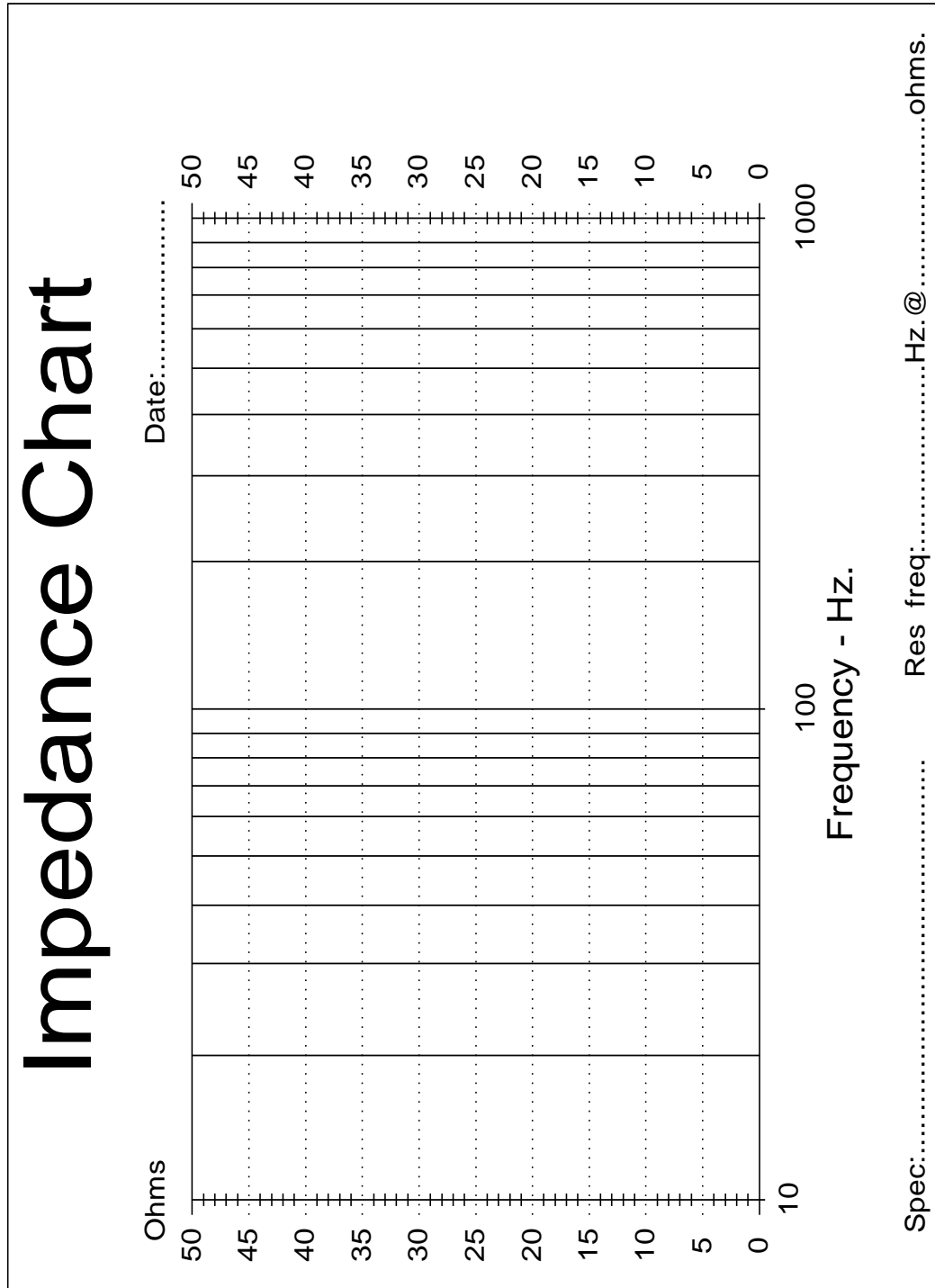Woofer Impedance Data Chart. (Right hand)



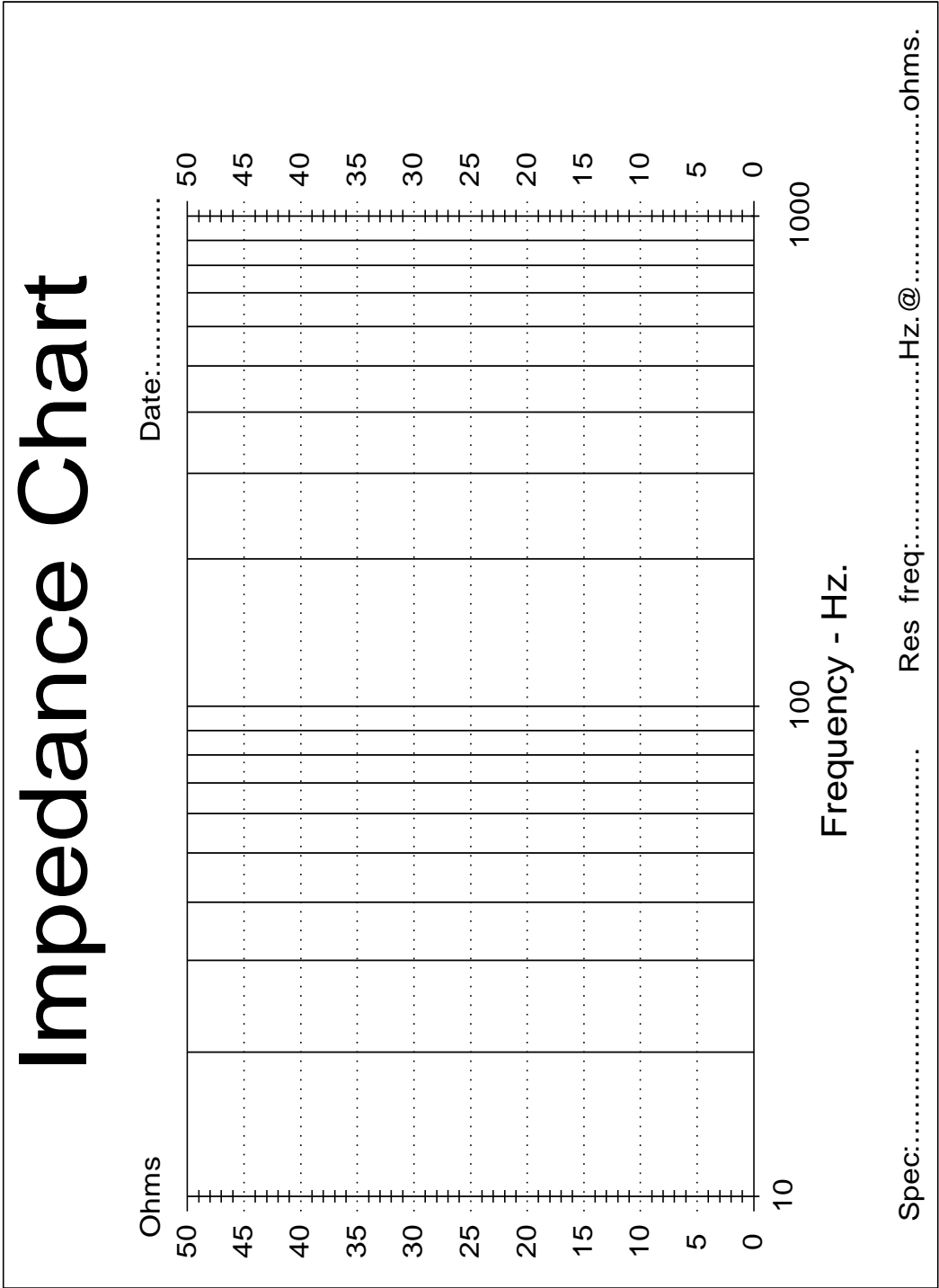Woofer Impedance Curve Chart. (Left hand)



Woofer Impedance Curve Chart. (Right hand)

Appendix A

TYPE : P/N : DATE :		
	LEFT HAND	RIGHT HAND
<u>Woofer parameters :</u> <div style="border: 1px solid black; border-radius: 10px; padding: 5px; display: inline-block; margin-bottom: 10px;"> <u>Crossover point:</u> Hz. </div> <div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> $Z_{fs} = \frac{V_s}{V_r} \frac{mV}{V}$ </div> <div style="width: 50%;"> R_e Ohms. F_s Hz. Z_{fs} Ohms. Z_{f3} Ohms. F_1 Hz. F_2 Hz. </div> </div> <u>Impedance Z:</u> L_o $Z_{f3} = .707 \times Z_{fs}$ F_1 & F_2 is the frequency of Z_{f3} above & below F_s .	<div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> = </div> <div style="width: 50%;"> Z_{fs} Ω $Z_{f3} = .707 \times \dots = \dots \Omega$ </div> </div>	<div style="display: flex; justify-content: space-between;"> <div style="width: 45%;"> = </div> <div style="width: 50%;"> Z_{fs} Ω $Z_{f3} = .707 \times \dots = \dots \Omega$ </div> </div>
<u>Speaker Q:</u> $r_0 = \frac{Z_{fs}}{R_e}$ $Q_{ts} = \frac{F_s}{F_1 - F_2} \times \frac{R_e}{Z_{fs}} \times \sqrt{r_0}$	$r_0 = \dots = \dots$ $\dots \times \dots \times \sqrt{\dots}$ $Q_{ts} = \dots$	$r_0 = \dots = \dots$ $\dots \times \dots \times \sqrt{\dots}$ $Q_{ts} = \dots$
Check F_s : ($\pm 1\%$) $F_s = \sqrt{F_1 \times F_2}$ Hz	$\sqrt{\dots \times \dots} = \dots$ Hz	$\sqrt{\dots \times \dots} = \dots$ Hz
Calculate $L_{ref} = R_e \times \sqrt{2}$ Find L_{ref} above F_s and record F_5 . (>300Hz.)	$\dots \times \sqrt{2} = \dots \Omega$ $F_5 = \dots$ Hz.	$\dots \times \sqrt{2} = \dots \Omega$ $F_5 = \dots$ Hz.
<u>Max Output.</u> $SPL = 10 \log(P) + S$ P = rms watts. S = sensitivity- dB@1w/1 m	$= 10 \log \dots + \dots$ $= \dots$ dB SPL.	$= 10 \log \dots + \dots$ $= \dots$ dB SPL.

Appendix A

$$C7 = \dots\dots\dots \mu F.$$

$$R4 = \dots\dots\dots \Omega.$$

$$F_5 = \dots\dots\dots \text{Hz. (see data chart)}$$

$$\text{Where } L_e = \frac{R_e}{2 \times \pi \times F_5} \times 10^3 = \dots\dots\dots \times 10^3 = \dots\dots\dots \text{mH.}$$

$$C7 = \frac{L_e}{R_e^2} \times 10^3 = \frac{\dots\dots\dots}{(\dots\dots\dots)^2} \times 10^3 = \dots\dots\dots \mu F.$$

$$R4 \text{ (Use a standard 5watt value close to } R_e. \text{)} = \dots\dots\dots \Omega.$$

Check the impedance curve as a reference
and aim to get a straight line)

Note: Use R4 as Z_w in the woofer crossover calculation chart if using an impedance equalizer.

Woofer Impedance Equalizer Calculation Chart.

$$\eta_{\text{eff}} = \frac{0.0953 \times (F_s^3 \times V_{as}) \times 10^{-6}}{Q_{es}} = \frac{0.0953 \times ((\dots\dots\dots)^3 \times \dots\dots\dots) \times 10^{-6}}{\dots\dots\dots} = \dots\dots\dots\%$$

$$Q_{es} = \frac{Q_{ms}}{(r_o - 1)} = \frac{\dots\dots\dots}{(\dots\dots\dots - 1)} = \dots\dots\dots$$

$$r_o = \frac{Z_{fs}}{R_e} = \dots\dots\dots = \dots\dots\dots \quad (\text{see data chart for } R_e, Z_{fs}, F_h, F_l)$$

$$Q_{ms} = \frac{F_s \times \sqrt{r_o}}{(F_1 - F_2)} = \frac{\dots\dots\dots \times \sqrt{\dots\dots\dots}}{\dots\dots\dots} = \dots\dots\dots$$

$$V_{as} = 1.15 \times \left(\left(\frac{F_{box}}{F_s} \right)^2 - 1 \right) \times V_{box} = 1.15 \times (\dots\dots\dots - 1) \times \dots\dots\dots$$

= $\dots\dots\dots$ liters

Woofer Relative Efficiency calculation chart.

Appendix A

TYPE : P/N : DATE :		
	LEFT HAND	RIGHT HAND
Midrange parameters : <div style="border: 1px solid black; border-radius: 10px; padding: 5px; width: fit-content; margin: 10px auto;"> Crossover point: L_oHz & H_iHz </div> $Z_{fs} = \frac{V_{s_r}}{V_r} \frac{mV}{V}$ Impedance Z:	R_e Ohms. F_s Hz. Z_{fs} Ohms. Z_{ml} Ohms. Z_{mh} Ohms. _____ = $Z_{fs} =$ Ohms. = _____ = $Z_{ml} =$ Ohms. M_{Lo} = _____ = $Z_{ml} =$ Ohms. M_{Hi} = _____ = $Z_{mh} =$ Ohms.	R_e Ohms. F_s Hz. Z_{fs} Ohms. Z_{ml} Ohms. Z_{mh} Ohms. _____ = $Z_{fs} =$ Ohms. = _____ = $Z_{ml} =$ Ohms. $Z_{ml} =$ Ohms.

Midrange Impedance Calculation Chart.

Parameters: $F_n =$ Hz

$R_3 =$ Ω

$L_6 =$ mH

$C_6 =$ μF

 $C_{ideal} = \frac{1}{2 \times \pi \times R_e \times F_n} \times 10^6 = \frac{10^6}{\quad} =$ uF

 $L_6 = \frac{1}{C_n \times (2 \times \pi \times F_n)^2} \times 10^3 = \frac{10^3}{\quad} =$ mH

 $R_3 = R_e =$ ohms.

F_n is the frequency of the notch you want to control and is usually equal to F_s .
 Calculate C_{ideal} , then choose the nearest standard value capacitor for C_n to enable a small enough coil to be wound (<6mH).

Midrange Notch Filter Calculation Chart.

Appendix A

TYPE : P/N : DATE :		
	LEFT HAND	RIGHT HAND
<u>Tweeter parameters :</u> <div style="border: 1px solid black; padding: 5px; margin: 10px 0; display: inline-block;"> <u>Crossover point:</u> Hz </div> $Z_{fs} = \frac{V_s}{V_r} \frac{mV}{V}$ <u>Impedance Z:</u>	R_e Ohms. F_s Hz. Z_{fs} Ohms. Z_t Ohms. _____ = $Z_{fs} =$ Ohms. $H_i =$ _____ = $Z_t =$ Ohms.	$.....$ Ohms. $.....$ Hz. $.....$ Ohms. $.....$ Ohms. _____ = $Z_{fs} =$ Ohms. $=$ _____ = $Z_t =$ Ohms.

Tweeter Impedance Calculation Chart.

Parameters: $F_n =$ Hz

$R_2 =$ Ω

$L_5 =$ mH

$C_5 =$ μF

$C_{ideal} = \frac{1}{2 \times \pi \times R_e \times F_n} \times 10^6 = \frac{10^6}{.....} =uF$

$L_5 = \frac{1}{C_n \times (2 \times \pi \times F_n)^2} \times 10^3 = \frac{10^3}{.....} =mH$

$R_2 = R_e =ohms.$

F_n is the frequency of the notch you want to control and is usually equal to F_s .
 Calculate C_{ideal} , then choose the nearest standard value capacitor for C_n to enable a small enough coil to be wound (<6mH).

Tweeter Notch Filter Calculation Chart.

Filter	1 st order	2 nd order		
	As calculated with the text book formulas. For higher orders multiply the standard values with the appropriate multiplier.	Butterworth	L/R	Bessel
C1		0.707	0.50	0.57
C4		0.707	0.50	0.57
L1		1.414	2.00	1.74
L4		1.414	2.00	1.74
		n th multipliers		

Table 1

Crossover Parts List.

+ = series connection. * = parallel connection.

Tweeter: crossover point =Hz.

C1 = μ F =@.....v@.....v

C5 = μ F =@.....v@.....v

C6 = μ F =@.....v@.....v

R1 = Ω = or

R2 = Ω =

L1 =mH

L5 =mH

Midrange: crossover point =&.....Hz.

C2 = μ F =@.....v@.....v

C3 = μ F =@.....v@.....v

C6 = μ F =@.....v@.....v

R3 = Ω =

L2 =mH

L3 =mH

L6 =mH

Woofer: crossover point =Hz.

C4 = μ F =@.....v@.....v

C7 = μ F =@.....v@.....v


L4 =mH

R4 = Ω =

Note: Use higher voltage rated caps on parallel connection.

Crossover Parts List.

Inductance Chart.

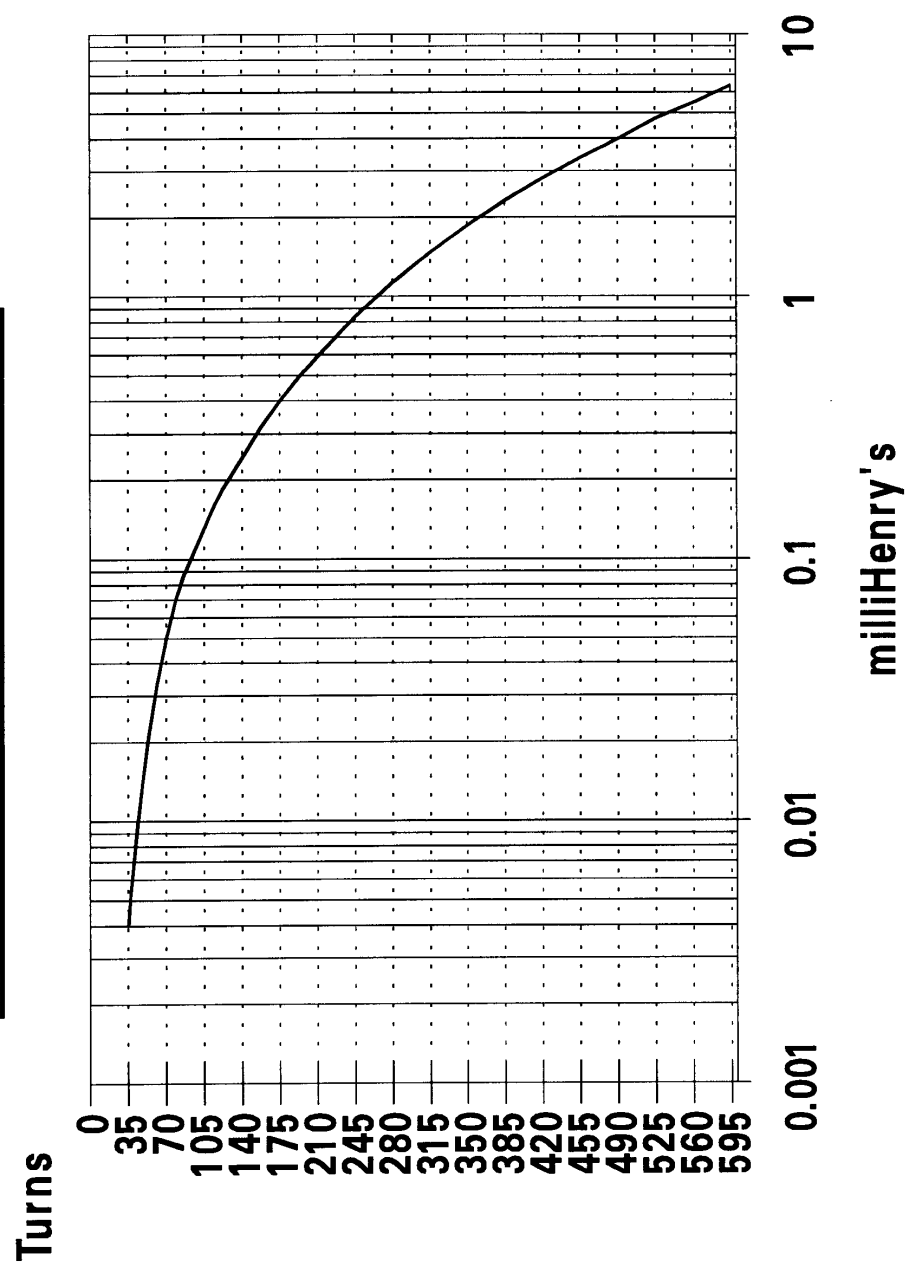

1mm enamelled copper wire.
38mm wide bobbin.(see fig 21)

