

Appendix A

Loudspeaker dimensions.	ii.
Loudspeaker parameters chart-L\H.	iii.
Loudspeaker parameters chart-R\H.	iv.
Woofers impedance curve chart-L\H.	v.
Woofers impedance curve chart-R\H.	vi.
Woofers parameters calculation chart.	vii.
Woofers crossover calculation chart	viii.
Tweeters parameters calculation chart.	ix.
Tweeters Zobel calculation chart.	x.
Tweeters Crossover network calculation chart.	xi.
Crossover parts list.	xii.
Inductance chart	xiii.
Crossover schematics	xiv.
Crossover layout	xv.

Loudspeaker Dimensions


Woofer		
Outside diameter	W_{diam}mm.
Woofer radius	R_wmm.
Magnet radius	r_wmm.
Woofer height	H_wmm.
Cone depth	W_{cone}mm.
Flange thickness	W_{flange}mm.
Flange width	W_{rebate}mm.
Cut-out diameter	W_{hole}mm.
Mounting screws		M.....
Tweeter		
Outside diameter	T_{diam}mm.
Magnet radius	R_tmm.
Cone depth	T_{cone}mm.
Flange thickness	T_{flange}mm.
Flange width	T_{rebate}mm.
Cut-out diameter	T_{hole}mm.
Mounting screws		M.....

FREQUENCY Hz.	V _S mvolts.	V _R volts.	IMPEDANCE Ohms.
10			
15			
20			
25			
30			
35			
40			
50			
60			
70			
80			
90			
100			
200			
300			
400			
500			
600			
700			
800			
900			
1000			
Resonant Frequency - F _s			


Woofer Impedance Data Chart. (Left hand)

FREQUENCY Hz.	V _S mvolts.	V _R volts.	IMPEDANCE Ohms.
10			
15			
20			
25			
30			
35			
40			
50			
60			
70			
80			
90			
100			
200			
300			
400			
500			
600			
700			
800			
900			
1000			
Resonant Frequency - F _s			


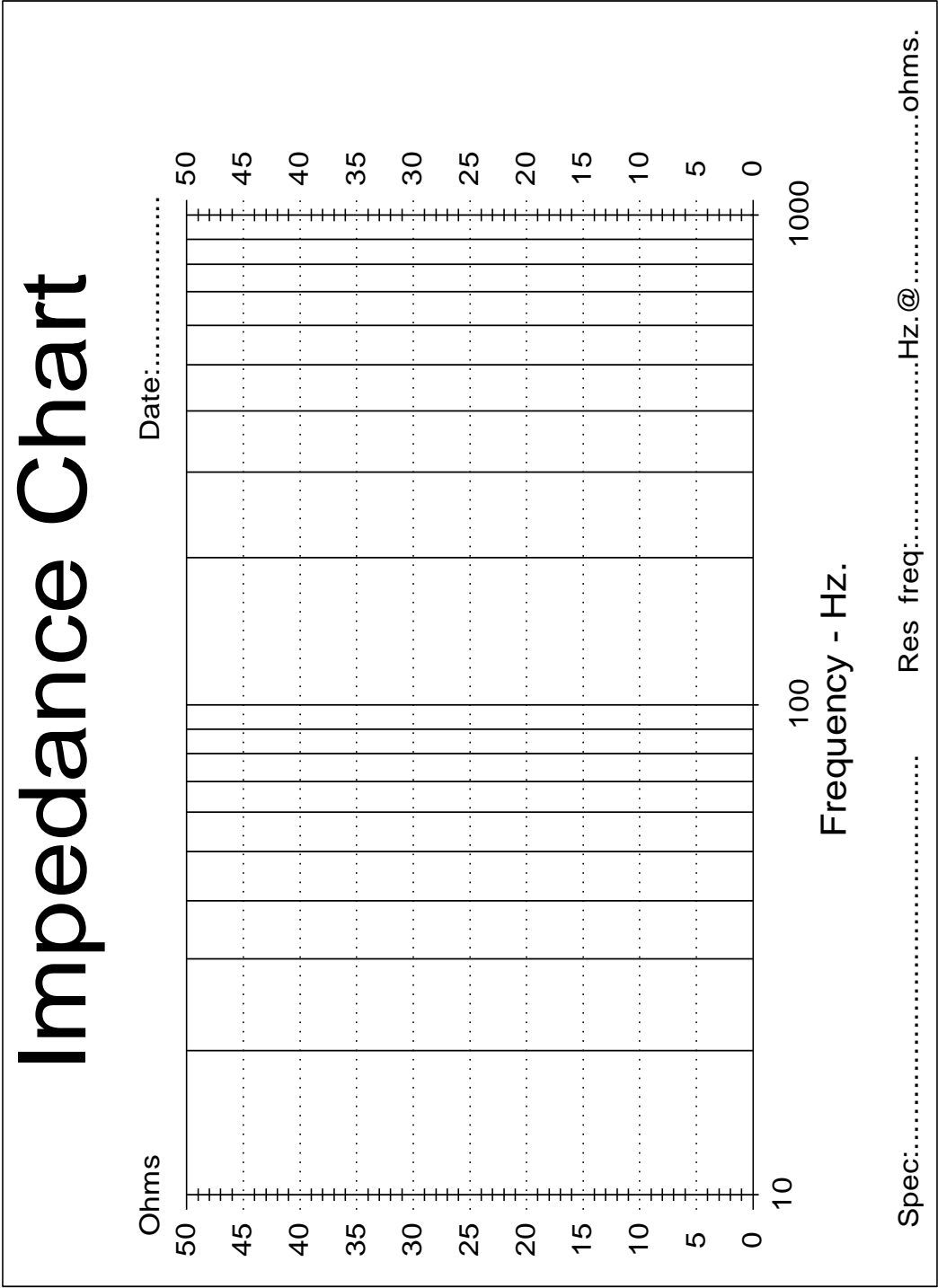
Woofer Impedance Data Chart. (Right hand)



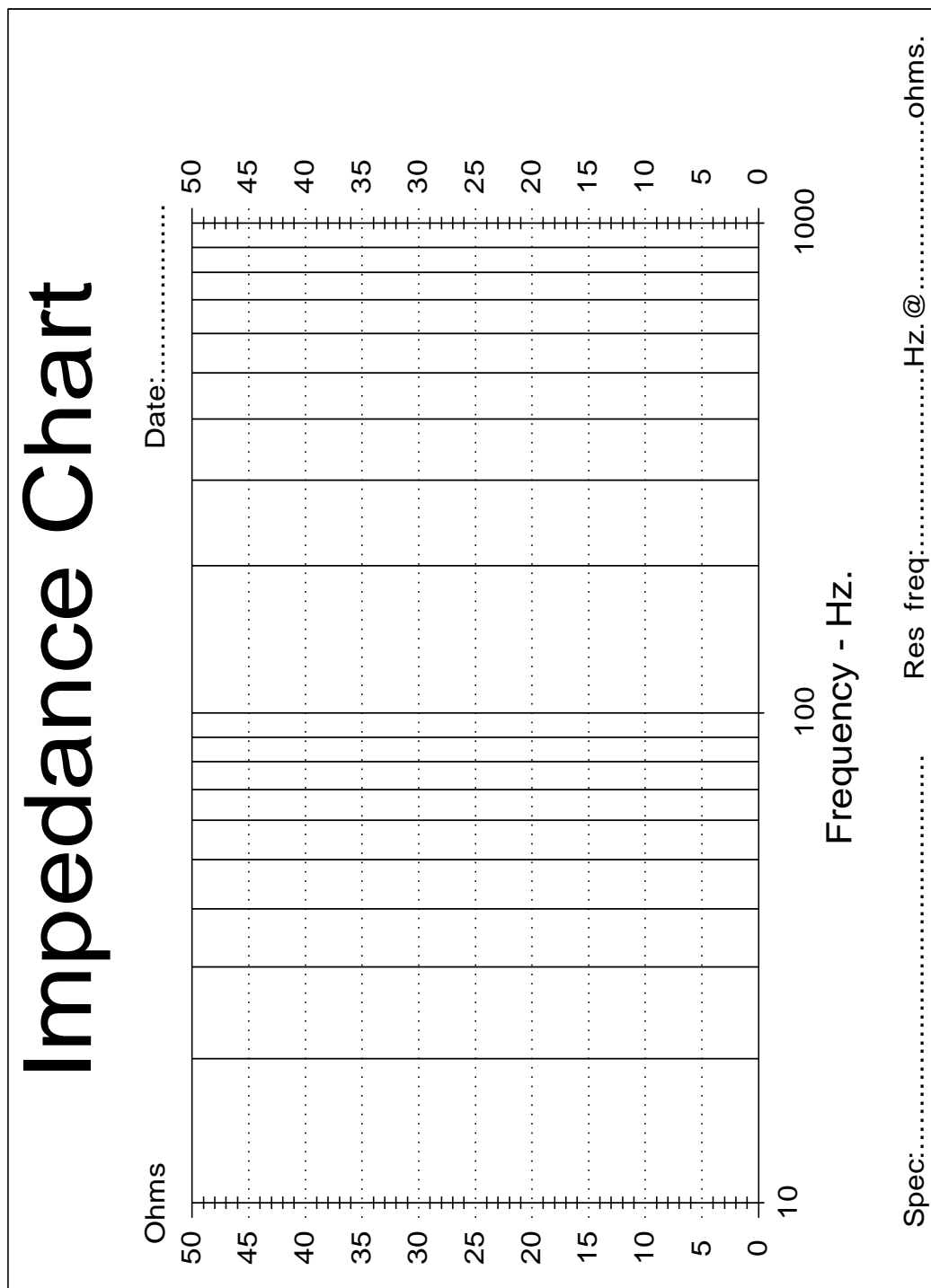Woofer Impedance Curve Chart. (Left hand)



Woofer Impedance Curve Chart. (Right hand)

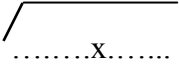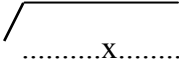TYPE :			P/N :			DATE :		
			LEFT HAND			RIGHT HAND		
Woofer parameters : <div style="border: 1px solid black; padding: 5px; display: inline-block;"> Crossover point: Hz. </div>								
R_e Ohms. F_s Hz. Z_{fs} Ohms. Z_{f3} Ohms. F_1 Hz. F_2 Hz.					 Ohms. Hz. Ohms. Ohms. Hz. Hz.		
$Z_{fs} = \frac{V_s}{V_r} \frac{mV}{V}$			_____ =			_____ =		
		 Ω		 Ω		
$Q_{ts} = \frac{F_s}{F_1 - F_2} \times \frac{R_e}{Z_{fs}}$		 x x		
$Z_{f3} = .707 \times Z_{fs}$ F_1 & F_2 is the frequency of Z_{f3} above & below F_s .			$Q_{ts} =$ $Z_{f3} = .707 \times \dots = \dots \Omega$			$Q_{ts} =$ $Z_{f3} = .707 \times \dots = \dots \Omega$		
Check F_s : ($\pm 1\%$) $F_s = \sqrt{F_1 \times F_2}$ Hz			x..... = Hz			x..... = Hz		
Calculate $L_{ref} = R_e \times \sqrt{2}$ Find L_{ref} above F_s and record F_5 (>300Hz.)			= x $\sqrt{2}$ = Ω $F_5 =$ Hz.			= x $\sqrt{2}$ = Ω $F_5 =$ Hz.		
Max Output. $SPL = 10 \log(P) + S$ $P =$ rms watts. $S =$ sensitivity- dB @ 1w/1 m			=10LOG.....+..... =.....dB SPL.			=10LOG.....+..... =.....dB SPL.		

Woofer Crossover Calculation Chart - Zobel/Butterworth.

Zobel Network:

Date:

$$R_5 = \dots\dots\dots \Omega$$

$$C_9 = \dots\dots\dots \mu F$$

$$R_e = \dots\dots\dots \Omega$$

$$F_5 = \dots\dots\dots \text{Hz.}$$

$$L_e = \dots\dots\dots \text{mH.}$$

$$L_e = \frac{R_e}{2 \times \pi \times F_5} = \frac{\dots\dots\dots}{2 \times \pi \times \dots\dots\dots} \times 10^3 = \dots\dots\dots \text{mH}$$

$$C_9 = \frac{L_e}{R_e^2} = \frac{\dots\dots\dots}{(\dots\dots\dots)^2} \times 10^3 = \dots\dots\dots \mu F$$

$$R_5 = R_e \text{ @5watt} = \dots\dots\dots \Omega$$

Crossover Network:Crossover point: $F_{10} = \dots\dots\dots \text{Hz.}$

$$L_4 = \dots\dots\dots \text{mH}$$

$$C_4 = \dots\dots\dots \mu F$$

$$\chi = \frac{\sqrt{2}}{2} = 0.707$$

$$\text{Frequency factor } \omega_{\text{cap}} = 2 \times \pi \times \sqrt[4]{3} \times F_{10} = 4.78 \times \dots\dots\dots = \dots\dots\dots$$

$$C_4 = \frac{\chi}{R_e \times \omega_{\text{cap}}} = \frac{0.707}{\dots\dots\dots \times \dots\dots\dots} \times 10^6 = \dots\dots\dots \mu F$$

$$\lambda = \sqrt{2} = 1.414$$

$$\text{Frequency factor } \omega_{\text{ind}} = \frac{2 \times \pi \times F_{10}}{\sqrt[4]{3}} = 4.78 \times \dots\dots\dots = \dots\dots\dots$$

$$L_4 = \frac{\lambda \times R_e}{\omega_{\text{ind}}} = \frac{1.414 \times \dots\dots\dots}{\dots\dots\dots} \times 10^3 = \dots\dots\dots \text{mH}$$

TYPE :		P/N :		DATE :	
	LEFT HAND		RIGHT HAND		
<p><u>Tweeter parameters :</u></p> <div style="border: 1px solid black; border-radius: 10px; padding: 5px; display: inline-block;"> <p>Crossover point:</p> <p>.....Hz.</p> </div> <p>R_e Ohms.</p> <p>F_s Hz.</p> <p>Z_{fs} Ohms.</p> <p>_____ = _____</p> <p>.....Ohms.</p>					
<p>$Z_{fs} = \frac{V_s}{V_r} \frac{mV}{V}$</p>					
<p><u>Zobel Parameters :</u></p> <p>Calculate: $r_o = \frac{Z_{fs}}{R_e}$</p> <p>Reference impedance :</p> <p>$R_{ref} = R_e \times \sqrt{r_o}$</p> <p>Record F_3 and F_4 where R_{ref} is above & below Z_{fs}.</p>	<p>$r_o = \text{_____} = \text{_____}$</p> <p>$R_{ref} = \text{_____} \times \sqrt{\text{_____}} = \text{_____}$</p> <p>$R_{ref} = \text{_____} \Omega$</p> <p>$F_3 = \text{_____} \text{ Hz.}$</p> <p>$F_4 = \text{_____} \text{ Hz.}$</p>		<p>$r_o = \text{_____} = \text{_____}$</p> <p>$R_{ref} = \text{_____} \times \sqrt{\text{_____}} = \text{_____}$</p> <p>$R_{ref} = \text{_____} \Omega$</p> <p>$F_3 = \text{_____} \text{ Hz.}$</p> <p>$F_4 = \text{_____} \text{ Hz.}$</p>		
<p>Check F_s : ($\pm 1\%$)</p> <p>$F_s = \sqrt{F_3 \times F_4} \text{ Hz}$</p>	<p>$\sqrt{\text{_____} \times \text{_____}} = \text{_____} \text{ Hz}$</p>		<p>$\sqrt{\text{_____} \times \text{_____}} = \text{_____} \text{ Hz}$</p>		
<p>Calculate $L_{ref} = R_e \times \sqrt{2}$</p> <p>Find L_{ref} above F_s and record F_5.(300-1000 Hz.)</p>	<p>$= \text{_____} \times \sqrt{2} = \text{_____} \Omega$</p> <p>$F_5 = \text{_____} \text{ Hz.}$</p>		<p>$= \text{_____} \times \sqrt{2} = \text{_____} \Omega$</p> <p>$F_5 = \text{_____} \text{ Hz.}$</p>		

Tweeter Zobel Calculation Chart - Zobel/Butterworth.

Zobel Network:

$$R_e = \dots\dots\dots\Omega \quad F_s = \dots\dots\dots\text{Hz.} \quad Z_{fs} = \dots\dots\dots\Omega$$

$$L_e = \dots\dots\dots\text{mH.} \quad Q_{ms} = \dots\dots\dots \quad Q_{es} = \dots\dots\dots$$

$$r_o = \dots\dots\dots \quad C_5 = \dots\dots\dots\mu\text{F} \quad C_6 = \dots\dots\dots\mu\text{F}$$

$$R_1 = \dots\dots\dots\Omega \quad R_2 = \dots\dots\dots\Omega \quad L_5 = \dots\dots\dots\text{mH}$$

Calculate:

$$F_3: \dots\dots\dots \quad F_4: \dots\dots\dots \quad (\text{From Speaker Data chart.})$$

$$Q_{ms} = \frac{F_s \times \sqrt{r_o}}{(F_3 - F_4)} = \frac{\dots\dots\dots \times \sqrt{\dots\dots\dots}}{\dots\dots\dots} = \dots\dots\dots$$

$$Q_{es} = \frac{Q_{ms}}{(r_o - 1)} = \frac{\dots\dots\dots}{(\dots\dots\dots - 1)} = \dots\dots\dots$$

$$R_{es} = \frac{Q_{ms} \times R_e}{Q_{es}} = \frac{\dots\dots\dots \times \dots\dots\dots}{\dots\dots\dots} = \dots\dots\dots$$

$$\text{Check: } R_{es} = Z_{fs} - R_e = \dots\dots\dots - \dots\dots\dots = \dots\dots\dots$$

$$L_{ces} = \frac{R_{es}}{2 \times \pi \times F_s \times Q_{ms}} = \frac{\dots\dots\dots}{2 \times \pi \times \dots\dots\dots \times \dots\dots\dots} = \dots\dots\dots$$

$$C_{mes} = \frac{Q_{ms}}{2 \times \pi \times F_s \times R_{es}} = \frac{\dots\dots\dots}{2 \times \pi \times \dots\dots\dots \times \dots\dots\dots} = \dots\dots\dots$$

$$F_5 = \dots\dots\dots\text{Hz} \quad (\text{From Speaker Data chart.})$$

$$L_e = \frac{R_e}{2 \times \pi \times F_5} = \frac{\dots\dots\dots}{2 \times \pi \times \dots\dots\dots} \times 10^3 = \dots\dots\dots\text{mH}$$

$$C_5 = \frac{L_e}{R_e^2} = \frac{\dots\dots\dots}{(\dots\dots\dots)^2} \times 10^3 = \dots\dots\dots\mu\text{F}$$

Tweeter cont.

$$L_5 = C_{mes} \times R_e^2 = \dots \times (\dots)^2 \times 10^3 = \dots \text{mH}$$

$$R_2 = \frac{R_e^2}{R_{es}} = \frac{(\dots)^2}{\dots} = \dots \Omega$$

$$C_6 = \frac{L_{ces}}{R_e^2} = \frac{\dots}{(\dots)^2} \times 10^6 = \dots \mu\text{F}$$

$$R_1 = R_e = \dots \Omega$$

Crossover Network:

Crossover point : F_{hi} Hz

$$C_1 = \dots \mu\text{F}$$

$$L_1 = \dots \text{mH.}$$

$$\chi = \frac{\sqrt{2}}{2} = 0.707$$

$$\text{Frequency factor } \omega_{cap} = 2 \times \pi \times \sqrt[4]{3} \times F_{hi} = ..8.27.. \times \dots = \dots$$

$$C_1 = \frac{\chi}{R_e \times \omega_{cap}} = \frac{0.707}{\dots \times \dots} \times 10^6 = \dots \mu\text{F}$$

$$\lambda = \sqrt{2} = 1.414$$

$$\text{Frequency factor } \omega_{ind} = \frac{2 \times \pi \times F_{hi}}{\sqrt[4]{3}} = ..8.27.. \times \dots = \dots$$

$$L_1 = \frac{\lambda \times R_e}{\omega_{ind}} = \frac{1.414 \times \dots}{\dots} \times 10^3 = \dots \text{mH}$$

Crossover Parts List.

+ = series connection. * = parallel connection.

Tweeter: crossover point =Hz.

C1 = μ F =@.....V@.....V

C5 = μ F =@.....V@.....V

C6 = μ F =@.....V@.....V

R1 = Ω =

R2 = Ω =

L1 =mH

L5 =mH

Woofer: crossover point =Hz.

C4 = μ F =@.....V@.....V

C9 = μ F =@.....V@.....V


L4 =mH

R5 = Ω =

Note: Use higher voltage caps on parallel connection.

Crossover Parts List.

Inductance Chart.

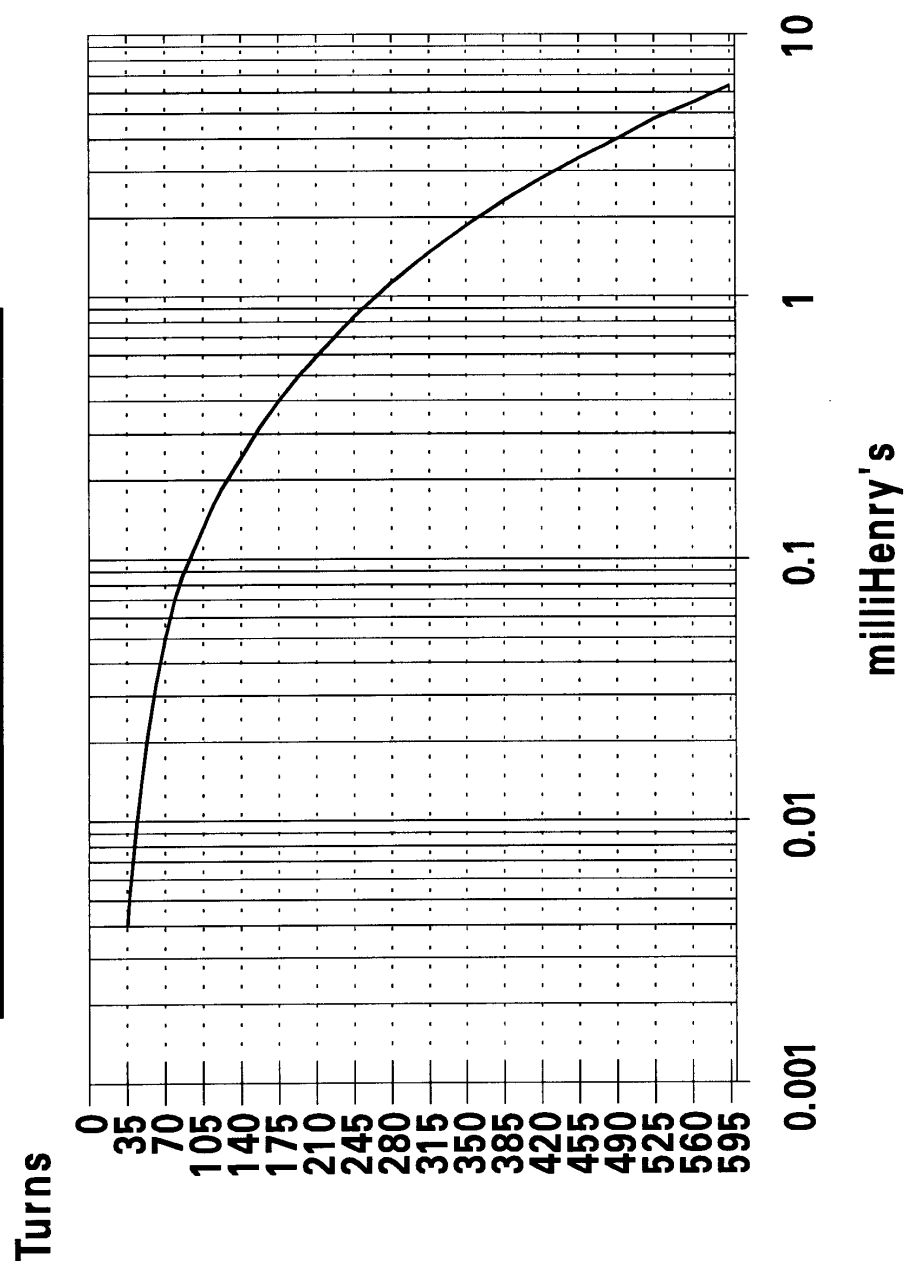

1mm enamelled copper wire.
38mm wide bobbin.(see fig 21)

Crossover network

Zobel network

